


Problem Set 1

Question 2

Shaurya Goyal

January 9, 2022

1

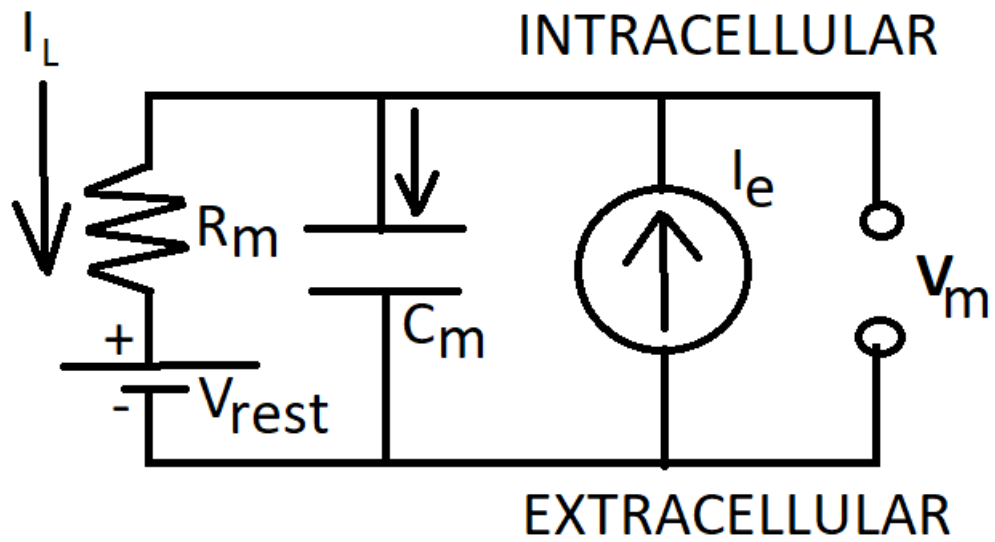

2

Specific membrane conductance $g_m = 1 \mu S/mm^2$

Radius of spherical neuron $r = 0.06 mm$

Surface area of a sphere $A = 4\pi r^2 = 144\pi \times 10^{-4} mm^2$

Total membrane conductance $G_m = g_m \times A = 144\pi \times 10^{-10} S$

Total membrane resistance $R_m = \frac{1}{G_m} = \frac{10^{10}}{144\pi} \Omega$

3

Specific membrane capacitance $c_m = 10 nF/mm^2$


Total membrane capacitance $C_m = c_m \times A = 144\pi \times 10^{-12} F$


4

Time constant $\tau_m = R_m C_m = 10^{-2} seconds$

5 MATLAB code in RCpassive.m

6

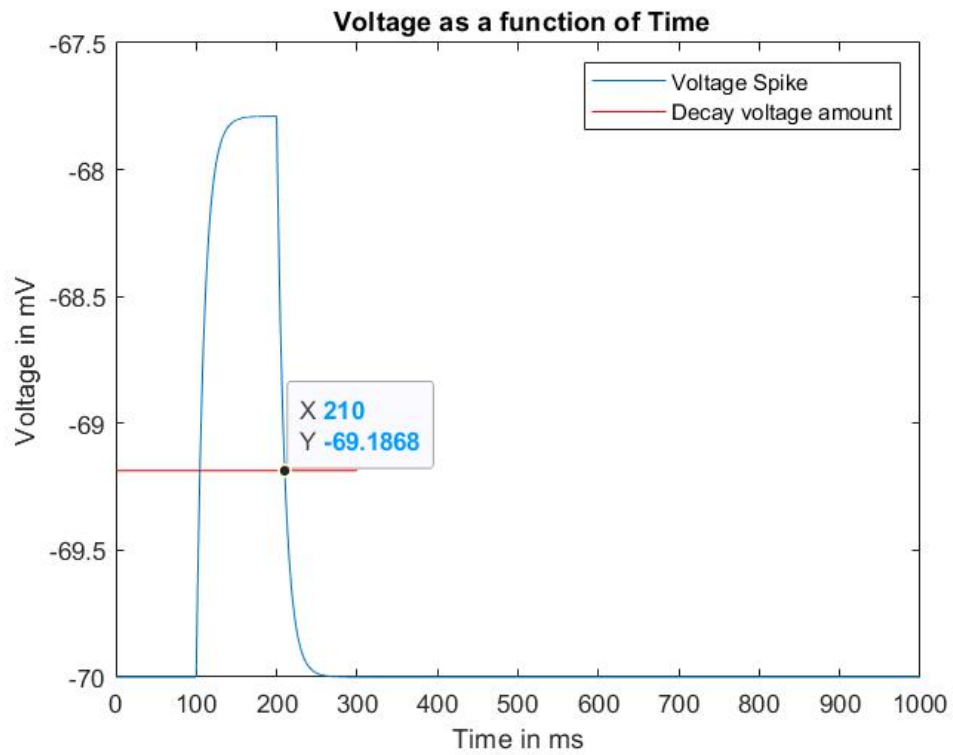

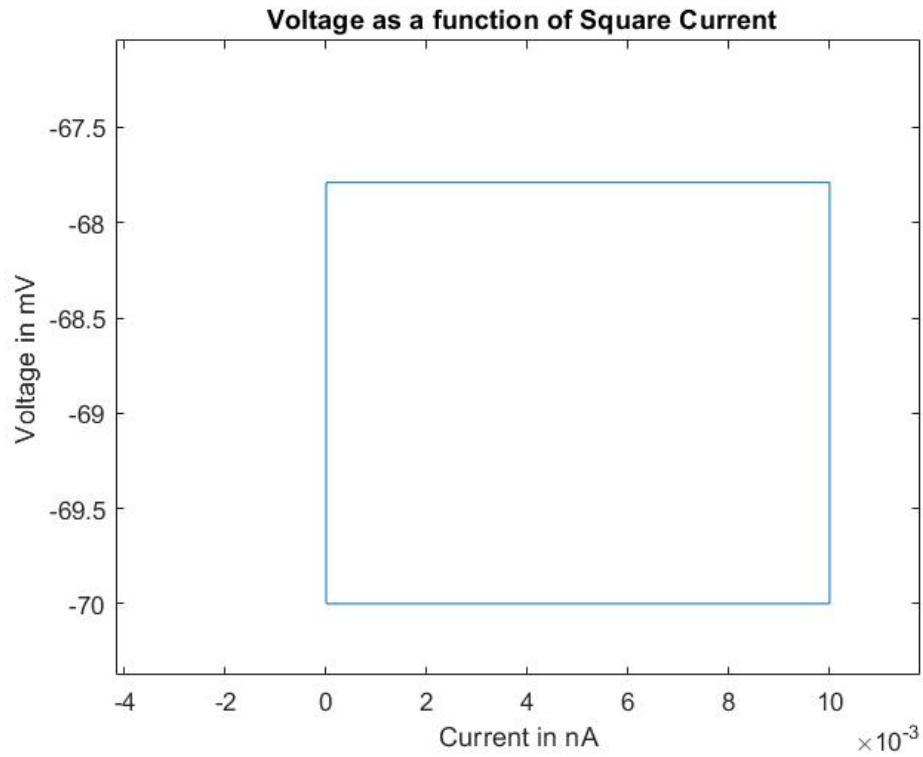

7

From plotting the decayed voltage amount (i.e $\frac{1}{e}$ times the total voltage change) in the "Voltage as a function of Time" graph in part 6, it is observed that the decayed voltage amount line intersects the the voltage graph at time = 210 *ms*

The neuron spikes at time = 200 *ms*

Therefore we can calculate the time constant from the graph as

$$\tau = \text{Time of intersection} - \text{Time of Spiking}$$

$$\tau = 10 \text{ ms}$$

8

This answer in part 7 obtained from simulation matches the time constant that was calculated analytically in part 4

9

The differential equation of the neuron is

$$V(t) + \tau_m \frac{dV(t)}{dt} = V_{rest} + R_m T_e$$

The equation can be rearranged and rewritten as

$$\frac{dV(t)}{dt} = \frac{V_{rest} + R_m T_e - V(t)}{\tau_m}$$

where, t is integrated from t_0 to t
 V is integrated from V_0 to $V(t)$

On separating the variables and integrating within the limits, we get

$$\log \frac{V_{rest} + R_m T_e - V(t)}{V_{rest} + R_m T_e - V_0} = - \left(\frac{t - t_0}{\tau_m} \right)$$

This can be rearranged to get the equation in the question

$$V(t) = V_{rest} + R_m I_e + (V_0 - V_{rest} - R_m I_e) \exp \left(\frac{t - t_0}{-\tau_m} \right)$$

□

10

At $t = t_0$, $V(t) = V_0$

On substituting these values of t and $V(t)$ in the final equation from part 9, we get,

$$V_0 = V_{rest} + R_m I_e + (V_0 - V_{rest} - R_m I_e) \exp\left(\frac{t_0 - t_0}{-\tau_m}\right)$$

It is observed that both the sides of the above equation cancel out.

Hence $V(t_0) = V_0$ satisfies the equation. \square

11

As $t \rightarrow \infty$, $\exp\left(\frac{t_0 - t_0}{-\tau_m}\right) \rightarrow 0$.

Therefore

$$V(t) \rightarrow V_{rest} + R_m I_e = V_\infty$$

\square

12

$I_e = 0.5 \text{ nA}$

$V(t) = -60 \text{ mV}$

The equation is rewritten in terms of time t as

$$t = \tau_m \ln\left(\frac{R_m I_e}{R_m I_e - V(t) + V_{rest}}\right)$$

On substituting the values, we get

$$t = 23.5 \text{ ms}$$

The steady state voltage formula is

$$\boxed{V_{\infty} = V_{rest} + R_m I_e}$$

On substituting the values, we get

$$\boxed{V_{\infty} = -58.9476 \text{ mV}}$$

13

The resistance in parallel (R_p) is added as follows to the original resistance R

$$\text{Combined membrane resistance } \boxed{R_m = \frac{R \times R_p}{R + R_p}}$$

Any addition of resistance in parallel causes the total resistance of the membrane to drop.

Since the time constant $\boxed{\tau_m \propto R_m}$

A decrease in membrane resistance causes the time constant to decrease i.e the time constant becomes faster.